

National Aviation University



Department of Electronics, Robotics, Monitoring and  
IoT Technologies

Course: "Fundamentals of Analog Electronics"

Experiment 4

**"Common Collector Amplifier"**

Prepared by prof. V. Ulansky



Kyiv

## OBJECTIVES

1. To measure the voltage and current gains of the CC amplifier.
2. To measure the input impedance of the CC amplifier.
3. To simulate the CC amplifier using MULTISIM software.


## EQUIPMENT

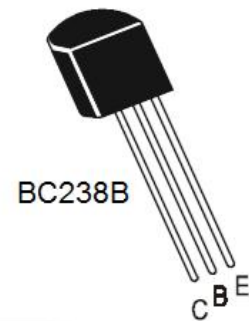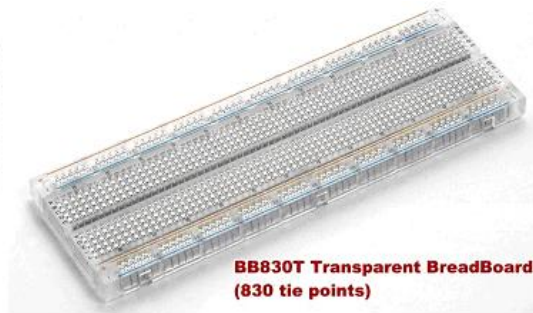1. Digital multimeter: Agilent 34401A
2. Solderless breadboard: BB830T
3. Oscilloscope: HAMEG HMO1024
4. Sinusoidal generator
5. Power Supply: 12V
6. BJT: BC238B
7. Resistors:  $2 \times 8.2 \text{ k}\Omega$ ,  $2 \times 1.2 \text{ k}\Omega$
8. Potentiometer:  $100 \text{ k}\Omega$
9. Capacitor:  $2 \times 10 \mu\text{F}$




## Theory

The circuit of a common-collector (CC) amplifier is shown in Fig. 1.

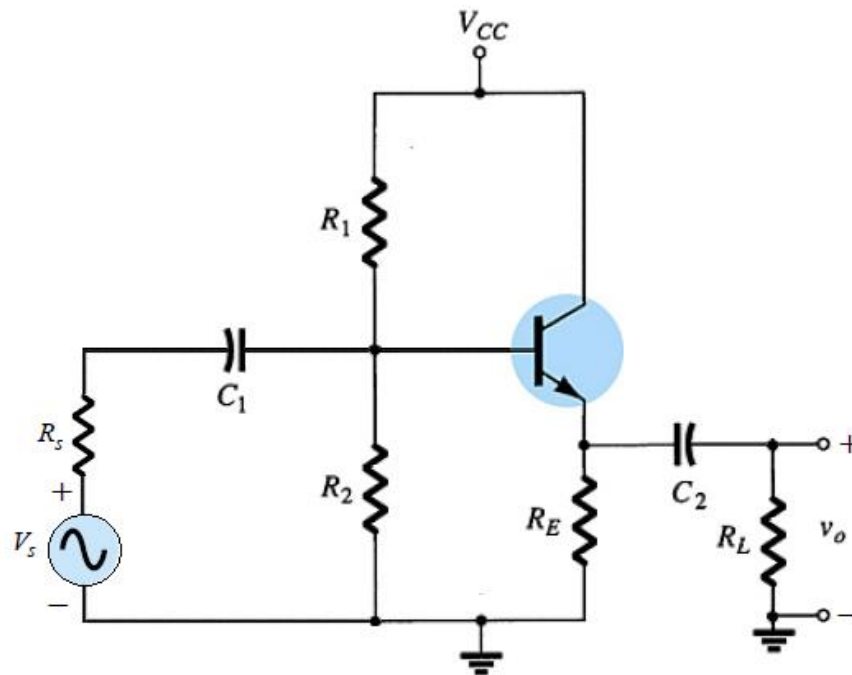


**Fig. 1** Common-collector amplifier circuit

The ac equivalent circuit of the CC amplifier is shown in Fig. 2. For converting the equivalent circuit of Fig. 2 into an equivalent electrical circuit, the transistor must be replaced by its small-signal model as shown in Fig. 3.

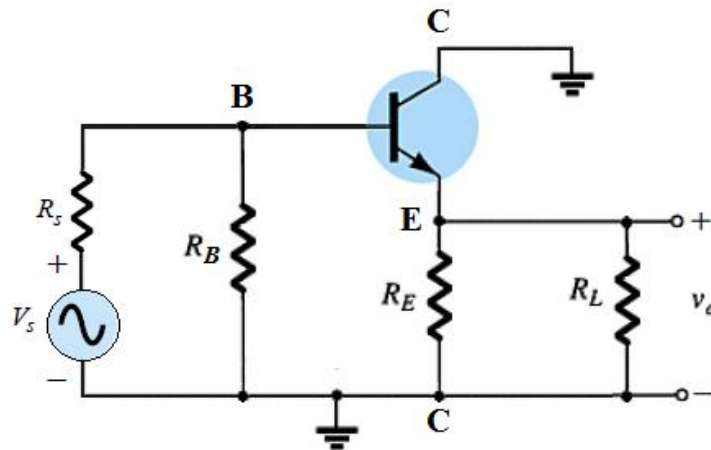


**Fig. 2** AC equivalent circuit of a CC amplifier

The complete CC small-signal model of the BJT with CE h-parameters has been substituted and the final network redrawn as shown in Fig. 4.

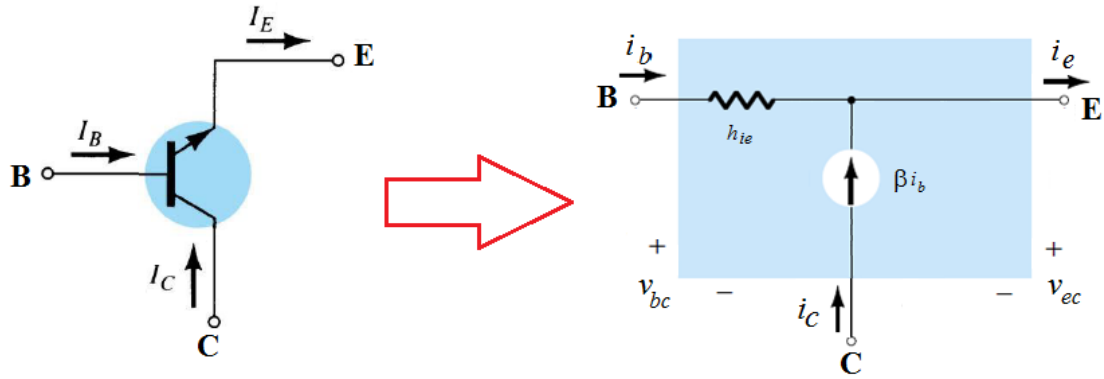

**Fig. 3** Replacement of transistor with a simplified small-signal model

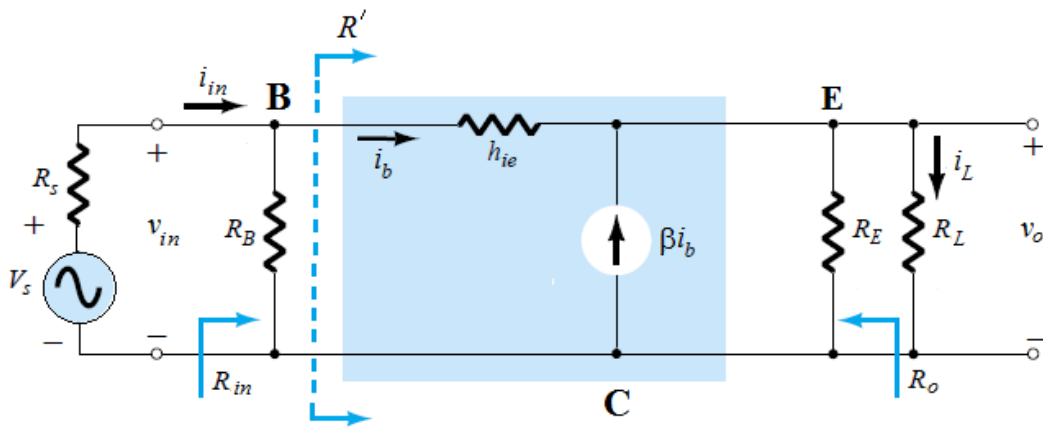

**Fig. 4** Small-signal model of the CC amplifier in mid frequency range

### Input Resistance, $R_{in}$

Let us begin by finding the resistance to the right of the dashed line in Fig. 4

$$R' = \frac{v_{in}}{i_B}$$

where

$$v_{in} = i_B h_{ie} + (1 + \beta) i_B (R_E \parallel R_L)$$

Now assuming that  $\beta$  is large ( $\beta + 1 \approx \beta$ ), we have

$$v_{in} = i_B (h_{ie} + \beta (R_E \parallel R_L))$$

Thus,

$$R' = h_{ie} + \beta(R_E \parallel R_L)$$

Now solving for  $R_{in}$  we have

$$R_{in} = R_B \parallel R' = R_B \parallel [\beta h_{ib} + \beta(R_E \parallel R_L)] = \frac{R_B [h_{ib} + (R_E \parallel R_L)]}{R_B/\beta + h_{ib} + (R_E \parallel R_L)}$$

If  $h_{ib} \ll R_E \parallel R_L$ , then  $h_{ib}$  can be neglected and

$$R_{in} = R_B \parallel [\beta(R_E \parallel R_L)]$$

### Current Gain, $A_i$

The current gain is defined as

$$A_i = \frac{i_L}{i_{in}}$$

where

$$i_B = i_{in} \frac{R_B}{R_B + h_{ie} + \beta(R_E \parallel R_L)}$$

$$i_L = \beta i_B \frac{R_E}{R_E + R_L}$$

and

$$i_{in} = i_B \frac{R_B + h_{ie} + \beta(R_E \parallel R_L)}{R_B}$$

Substituting  $i_L$  and  $i_{in}$  into equation for  $A_i$ , gives

$$A_i = \beta i_B \frac{R_E}{R_E + R_L} \bigg/ i_B \frac{R_B + h_{ie} + \beta(R_E \parallel R_L)}{R_B} = \frac{\beta R_E R_B}{(R_E + R_L)(R_B + h_{ie} + \beta(R_E \parallel R_L))}$$

and finally

$$A_i = \frac{R_E R_B}{(R_E + R_L) \left[ R_B / \beta + h_{ib} + (R_E \parallel R_L) \right]} \quad (1)$$

Equation (1) is the general expression for current gain. If  $h_{ib} \ll R_E \parallel R_L$ , then

$$A_i = \frac{\beta R_E R_B}{(R_E + R_L) \left[ R_B + \beta (R_E \parallel R_L) \right]}$$

If  $R_B \ll \beta (R_E \parallel R_L)$ , then

$$A_i \approx \frac{\beta R_E R_B}{(R_E + R_L) \left( \beta (R_E \parallel R_L) \right)} = \frac{\beta R_E R_B (R_E + R_L)}{(R_E + R_L) \beta R_E R_L} = \frac{R_B}{R_L}$$

Note that the current gain is positive for the CC amplifier, since  $i_{in}$  is in phase with  $i_L$ .

### Voltage Gain, $A_V$

We find the voltage gain from the gain impedance formula, input resistance, and the current gain:

$$A_V = A_i \frac{R_L}{R_{in}} \quad (2)$$

$$R_{in} = \frac{R_B (h_{ib} + R_E \parallel R_L)}{R_B / \beta + h_{ib} + R_E \parallel R_L}$$

(3)

$$A_i = \frac{\beta R_E R_B}{(R_E + R_L) \left( R_B + h_{ie} + \beta (R_E \parallel R_L) \right)} \quad (4)$$

Substituting (3) and (4) into 2 gives

$$A_V = \frac{R_E R_B R_L}{(R_E + R_L) \left[ R_B / \beta + h_{ib} + (R_E \parallel R_L) \right]} \times \frac{\left[ R_B / \beta + h_{ib} + (R_E \parallel R_L) \right]}{R_B \left[ h_{ib} + (R_E \parallel R_L) \right]}$$

and finally


$$A_V = \frac{R_E \parallel R_L}{h_{ib} + (R_E \parallel R_L)}$$

Since  $h_{ib}$  is usually small compared to  $R_E \parallel R_L$ , we can approximate the voltage gain as

$$A_V \approx 1$$


### Output Resistance, $R_O$

For finding  $R_O$  we shall use the CC equivalent circuit of the BJT with the CB  $h$ -parameter  $h_{ib}$  as shown in Fig. 5.

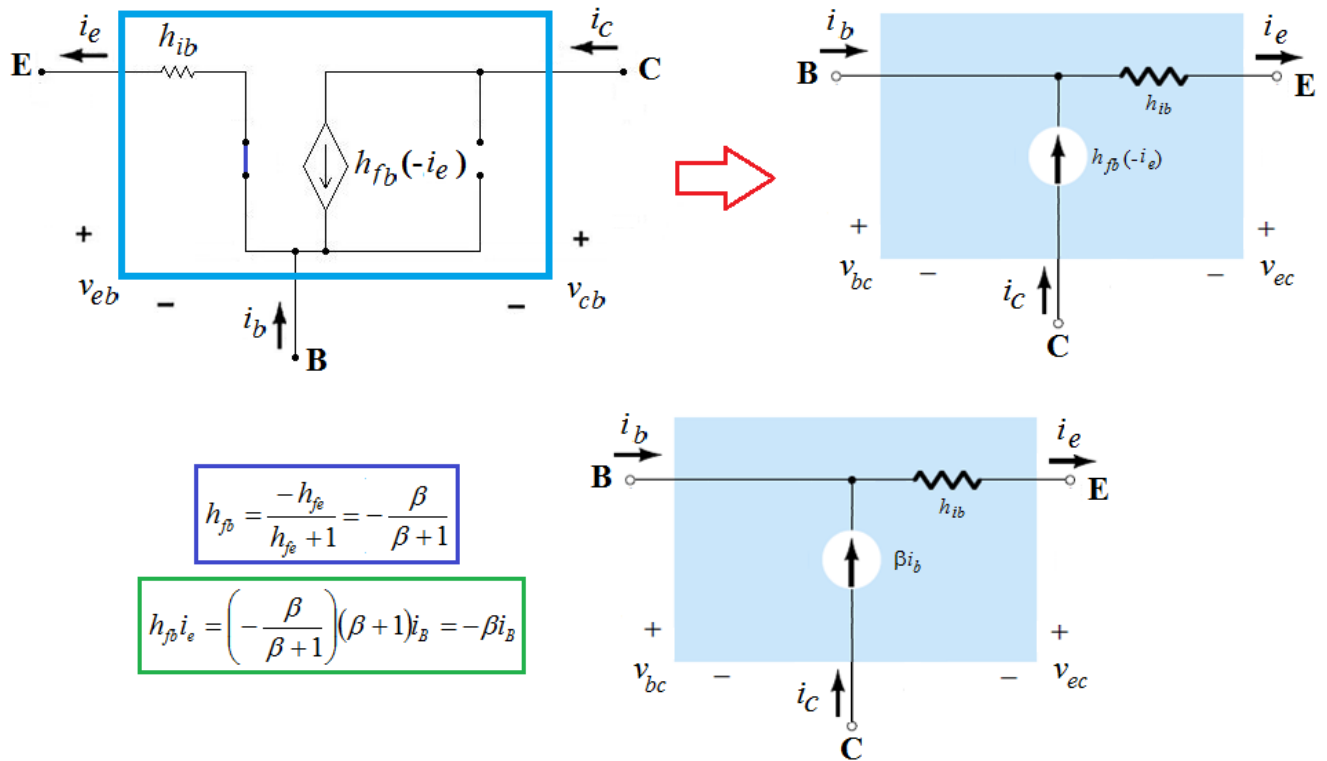


**Fig. 5** CC small-signal model of a BJT with CB small-signal parameter  $h_{ib}$

The small-signal equivalent circuit of the CC amplifier is shown in Fig. 6.

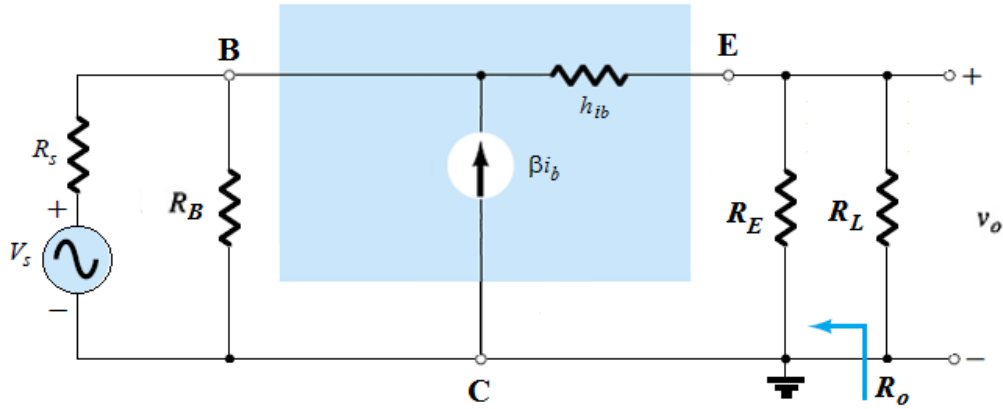

**Fig. 6** CC amplifier small-signal equivalent circuit

The output resistance is determined with assumption that  $R_L = \infty$ . In this case we can represent output current by an ideal current source,  $i_o$ , with infinity internal resistance. The input ac source must be set to 0. The corresponding small-signal model is shown in Fig. 7.

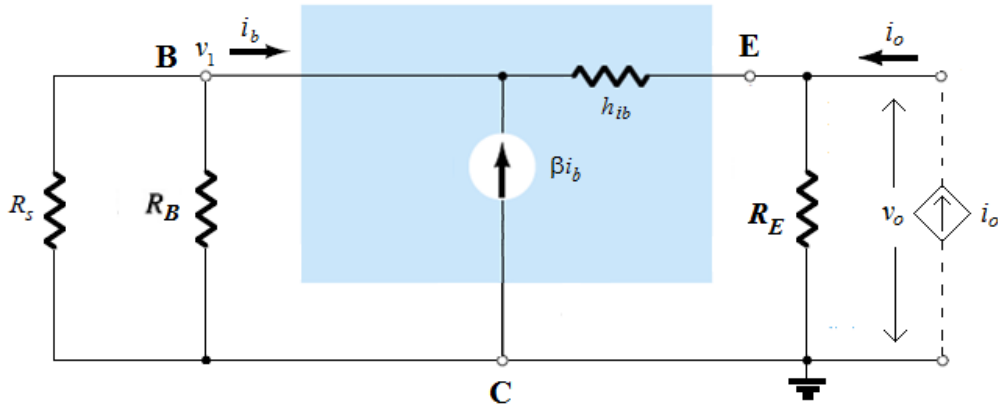

**Fig. 7** Small-signal model for finding output resistance of the CC amplifier

We write the following equations for the circuit:

$$i_b = \frac{0 - v_1}{R_s \parallel R_B} = -\frac{v_1}{R_s \parallel R_B} \quad (5)$$

$$v_1 - v_o = (1 + \beta)h_{ib}i_b \quad (6)$$

$$i_o = \frac{v_o}{R_E} + \frac{v_o - v_1}{h_{ib}} \quad (7)$$

From Eq. (5) and Eq. (6) we find  $v_o$



$$\begin{aligned}
v_1 &= -i_b(R_s \parallel R_B) \\
v_o &= v_1 - (1 + \beta)i_b h_{ib} = -i_b(R_s \parallel R_B) - (1 + \beta)i_b h_{ib} \\
v_o &= -i_b[(R_s \parallel R_B) + (1 + \beta)h_{ib}] \tag{8}
\end{aligned}$$

Substituting  $v_1 - v_o$  and  $v_o$  from Eq. (6) and Eq. (8) into Eq. (7), gives

$$i_o = -\frac{i_b}{R_E} [(R_s \parallel R_B) + (1 + \beta)h_{ib}] - \frac{(1 + \beta)i_b h_{ib}}{h_{ib}} = -i_b \left\{ \frac{1}{R_E} [(R_s \parallel R_B) + (1 + \beta)h_{ib}] + 1 + \beta \right\} \tag{9}$$

The output resistance of the CC configuration is

$$R_o = \frac{v_o}{i_o} = \frac{-i_b [(R_s \parallel R_B) + (1 + \beta)h_{ib}]}{-i_b \left\{ \frac{1}{R_E} [(R_s \parallel R_B) + (1 + \beta)h_{ib}] + 1 + \beta \right\}} = \frac{R_E [(R_s \parallel R_B) + (1 + \beta)h_{ib}]}{(R_s \parallel R_B) + (1 + \beta)h_{ib} + (1 + \beta)R_E} = \frac{R_E \left[ h_{ib} + \frac{(R_s \parallel R_B)}{\beta + 1} \right]}{R_E + h_{ib} + \frac{R_s \parallel R_B}{\beta + 1}}$$


Using approximation  $\beta + 1 \approx \beta$ , we have

$$R_o = \frac{R_E \left( h_{ib} + \frac{R_s \parallel R_B}{\beta} \right)}{R_E + h_{ib} + \frac{R_s \parallel R_B}{\beta}} = R_E \left\| \left( h_{ib} + \frac{R_s \parallel R_B}{\beta} \right) \right.$$

## PROCEDURE

1. Construct the CC amplifier circuit (see Fig. 8) on the solderless breadboard.
2. Turn on 12 V power supply.
3. Adjust the FREQUENCY control of signal generator so the output is 1 kHz sinusoidal waveform.
4. Adjust the 100 k $\Omega$  potentiometer ( $R_s$ ) fully counterclockwise (thus making it 0).
5. Adjust the amplitude of the generator output voltage so that the amplifier output voltage amplitude  $V_o$  is 1 V.
6. Measure the voltage amplitude going from the generator into the amplifier ( $V_i$ ). Record the voltage measurement.

7. Use the formula  $A_V = V_O/V_i$  to calculate the voltage gain. Record the voltage gain calculation.
8. Measure the rms current flowing from the generator into the amplifier ( $I_{i,rms}$ ). Record the input current measurement.
9. Measure the rms current flowing through the 1-k $\Omega$  load resistor ( $I_{L,rms}$ ). Record the load current measurement.
10. Use the formula  $A_I = I_{L,rms}/I_{i,rms}$  to calculate the current gain. Record the current gain calculation.
11. Readjust the 100 k $\Omega$  potentiometer ( $R_s$ ) so the amplifier output voltage amplitude is 0.5 V.
12. Turn off the power supply, and measure the resistance between terminals 1 and 2 of the 100 k $\Omega$  potentiometer ( $R_s$ ). Record this resistance value. It is equal to the amplifier input resistance  $R_{in}$ .
13. Use the formula  $I_{L,rms} = V_O/(\sqrt{2}R_L)$ , and the values of  $V_O$  (1 V) and  $R_L$  (1 k $\Omega$ ) to calculate the output current. Record your current calculation
14. Using the formula  $I_{i,rms} = V_i/(\sqrt{2}R_{in})$ , and the values of  $V_i$  (step 6) and  $R_{in}$  (step 12) that you recorded earlier to calculate the input rms current. Record the input current calculation.
15. Use the formula  $A_P = A_V A_I$  to calculate the power gain of the amplifier. Record the power gain calculation.

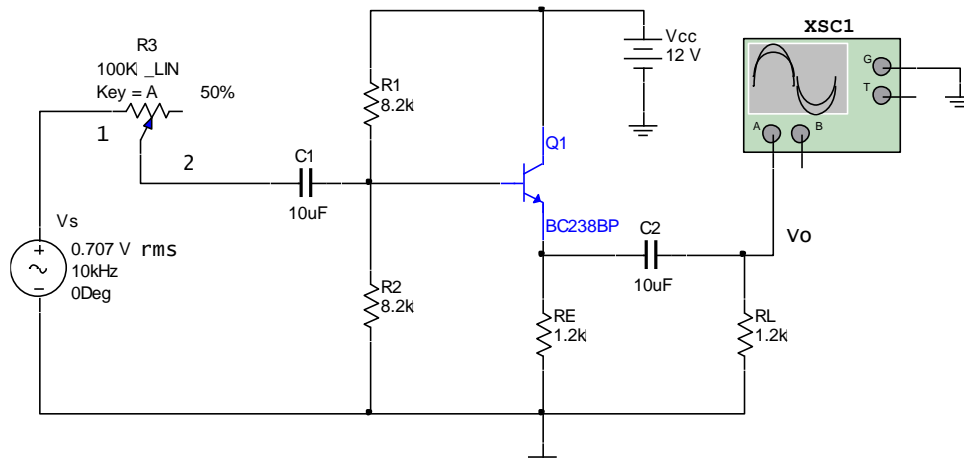

**Fig. 8** Experimental CC amplifier circuit diagram

## Reference

1. A.S. Sedra and K.S. Smith, "Microelectronic circuits", 5<sup>th</sup> ed., New York: Oxford University Press, 2004, 1283 p.