

National Aviation University  
Department of Electronics, Robotics, Monitoring and  
IoT Technologies



Course: “Analog and Digital Instrumentation”

## Experiment 6

**“Digital to analog converter using  $R-2R$  ladder”**

**«Цифро-аналоговий перетворювач з використанням резистивної матриці  $R-2R$ »**

Prepared by Prof. V. Ulansky


Kyiv 2020

## LEARNING OBJECTIVE

- To observe and measure the performance of a 4-bit R-2R digital to analogue converter.

## Introduction

A digital to analogue converter (DAC) is a device that outputs a voltage proportional to an input binary number. Such a device is frequently required in applications where a digital computer must generate a signal that has an influence on the ‘real’ world. Real world signals are continuously variable – i.e., analogue signals – whereas signals within a computer have a finite number of values – i.e., discrete signals. A DAC is used to perform the necessary conversion. Figure 1 shows the basic arrangement of a DAC using an R-2R ladder.

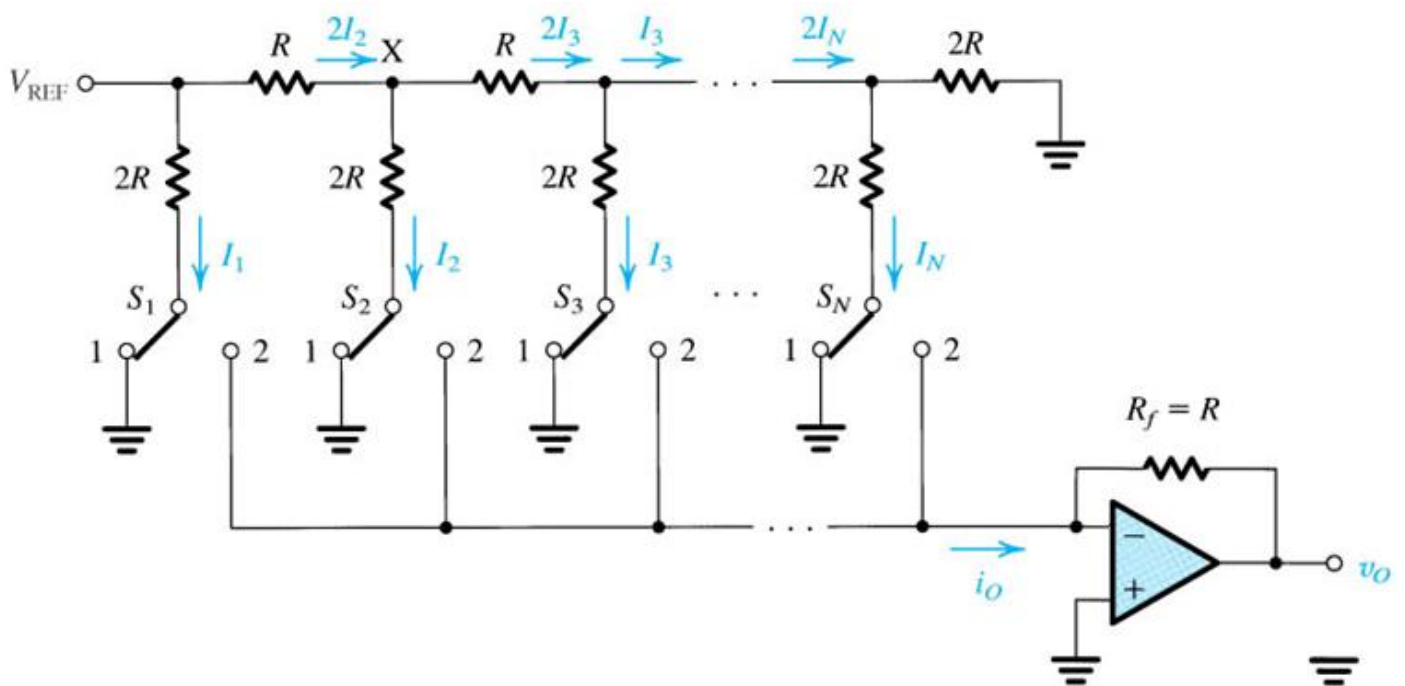

**Figure 1:** The basic circuit configuration of a DAC utilizing an R-2R ladder network

Because of the small difference in resistance values, this network is usually preferred to the binary-weighted scheme, especially for  $N > 4$ . Operation of the R-2R ladder is straightforward. First, it can be shown, by starting from the right and working toward the left, that **the resistance to the right of each ladder node, such as that labeled X, is equal to 2R.** Thus the current flowing to the right, away from each node, is equal to the

current flowing downward to ground, and twice that current which flows into the node from the left side. It follows that

$$I_1 = 2I_2 = 4I_3 = \dots = 2^{N-1} \times I_N$$

Thus, as in the binary-weighted resistive network, the currents controlled by the switches are binary weighted (*Таким чином, як і в резистивному ланцюгу з двійковим зважуванням, струми, керовані перемикачами, зважуються двійково*).

The output current  $i_o$  will therefore be given by

$$i_o = \frac{V_{REF}}{2R} b_1 + \frac{V_{REF}}{2R \times 2} b_2 + \dots + \frac{V_{REF}}{2R \times 2^{N-1}} = \frac{V_{REF}}{R} \left( \frac{b_1}{2^1} + \frac{b_2}{2^2} + \dots + \frac{b_N}{2^N} \right) = \frac{V_{REF}}{R} D \quad (1)$$

where  $D$  is the digital word.


And the output voltage  $v_o$  is determined as

$$v_o = -i_o R \quad (2)$$


The circuit of Fig. 1 was simulated for two binary words  $1010_2 = 10_{10}$  and  $1111_2 = 15$  as shown in Fig. 2. Using Equations (1) and (2) we find for the binary word  $1010_2$

$$i_o = \frac{V_{REF}}{R} \left( \frac{b_1}{2^1} + \frac{b_2}{2^2} + \dots + \frac{b_N}{2^N} \right) = \frac{16}{1k\Omega} \left( \frac{1}{2^1} + \frac{0}{2^2} + \frac{1}{2^3} + \frac{0}{2^4} \right) = 10\text{mA}$$
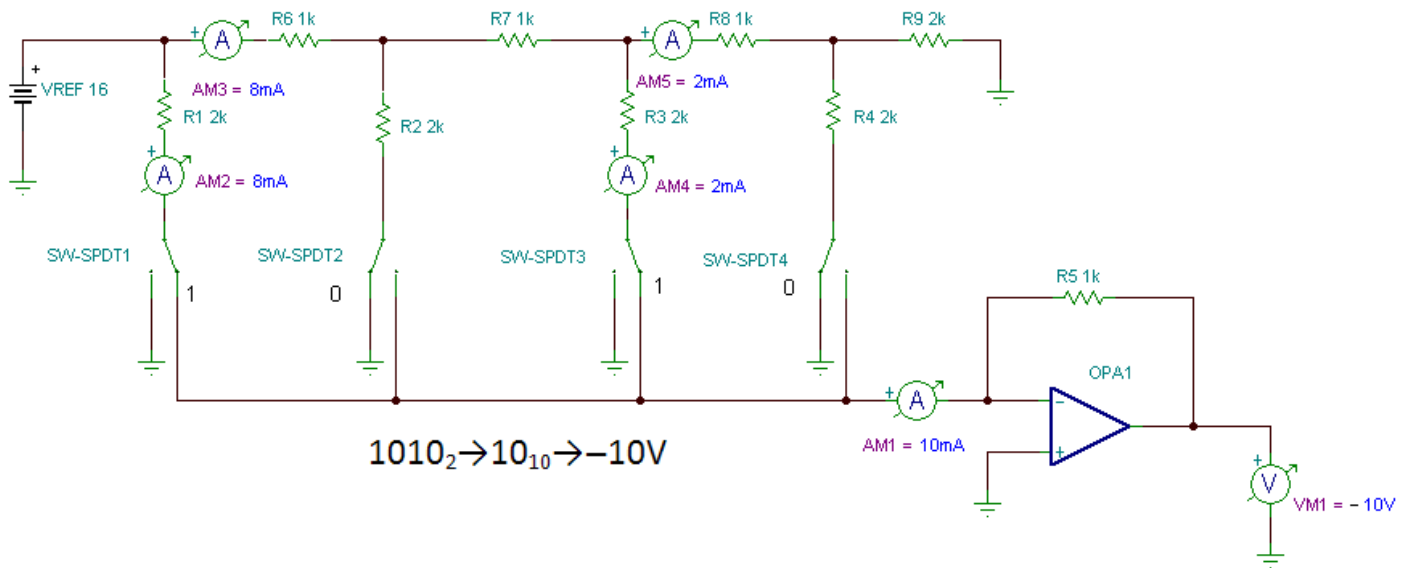
$$v_o = -i_o R = -(10\text{mA}) \times (1k\Omega) = -10\text{V}$$



(a)

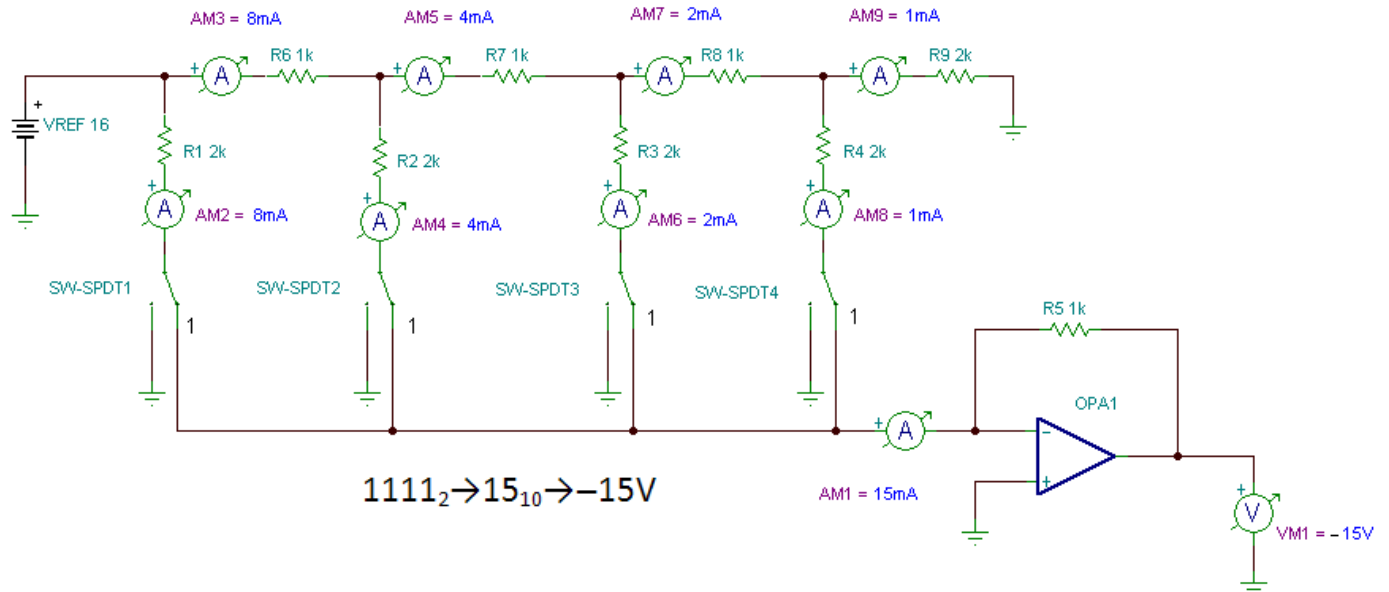

(b)

**Figure 2:** Simulation of the 4-bit DAC using an  $R$ - $2R$  ladder network

Analogically, we calculate  $i_o$  and  $v_o$  for the digital word  $1111_2$

$$i_o = \frac{V_{\text{REF}}}{R} \left( \frac{b_1}{2^1} + \frac{b_2}{2^2} + \dots + \frac{b_N}{2^N} \right) = \frac{16}{1\text{k}\Omega} \left( \frac{1}{2^1} + \frac{1}{2^2} + \frac{1}{2^3} + \frac{1}{2^4} \right) = 15\text{mA}$$

$$v_o = -i_o R = -(15\text{mA}) \times (1\text{k}\Omega) = -15\text{V}$$

As seen from Fig. 2, the simulated DAC circuit has the same voltages and currents as those calculated by Equations (1) and (22).

## EQUIPMENT

1. Digital multimeter Agilent 34401A
2. Solderless breadboard BB830T
3. Two power supplies:  $\pm 18\text{V}$ .
4. Power supply 16 V.
5. Resistors:  $4 \times 1.0 \text{ k}\Omega$ ,  $5 \times 2.0 \text{ k}\Omega$
6. 741 operational amplifier.




## PROCEDURE


The pin connections for the 8 pin DIP package  $\mu\text{A}741$  op-amp are given in Fig. 3. Throughout this experiment use the external DC Power Supplies with **+18V**, **0**, **-18V** jacks. The initial location of the  $\mu\text{A}741$  chip and connections to **+18V**, **0**, **-18V** terminals of the power supply are shown in Fig. 4.

To use the Power Supplies:

- Turn the Power Supplies ON. This will set both positive and negative power sources respectively to **+18V** and **-18V**. Measure these voltages with digital multimeter.

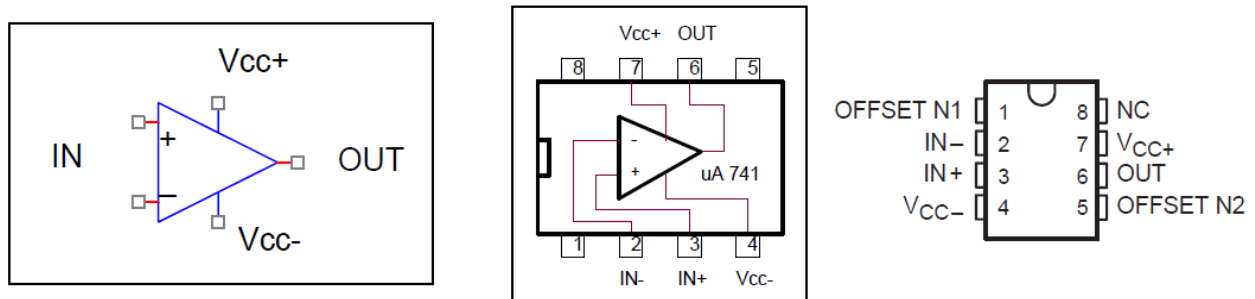

**Figure 3:** Symbol for a basic op-amp (a), the  $\mu\text{A}741$  op-amp package (b)

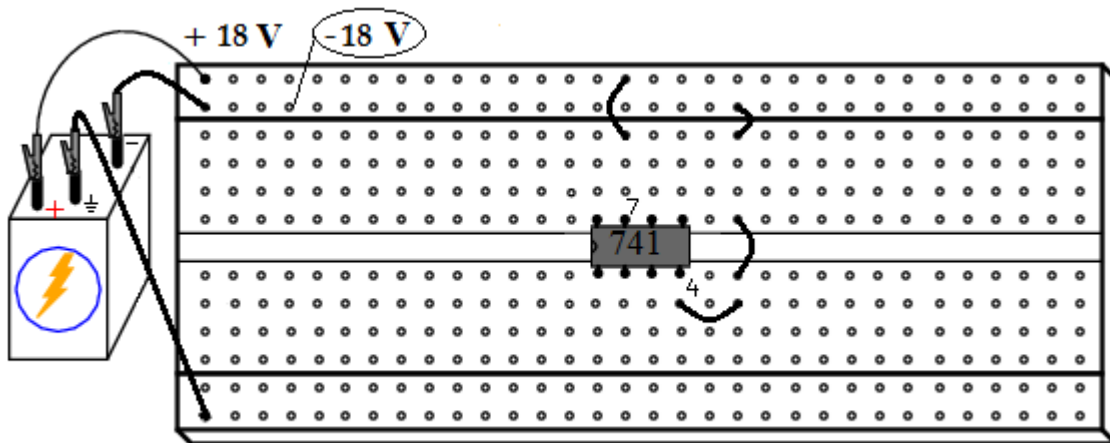

**Figure 4:** Initial location of uA741 chip on the solderless breadboard

- Turn the Power Supplies OFF before connecting to the circuits.
- Connect the **+18V** terminal of the Power Supply to the  $V_{CC}^+$  of your circuit as shown in Fig. 4. Connect the **-18V** terminal of the Power Supply to the  $V_{CC}^-$  of your circuit as shown in Fig. 4. Connect the **COM** terminal of the Power Supplies to the ground of your circuit as shown in Fig. 4.

1. Build the circuit with  $R = 1.0 \text{ k}\Omega$  and  $2R = 2.0 \text{ k}\Omega$ . Use wire links for D0-D3 to allow switching between LOW and HIGH.
2. Set  $V_{REF}$  to **16** volts.
3. Apply power to the circuit by turning on the  $\pm 18 \text{ V}$  power supplies.
4. For each given switch combination, measure and record the output voltage  $V_o$ .
5. Plot the results on the graph sheet.
6. Calculate the maximum % linearity error for the DAC from the plotted results.

$$E\% = 100\% \times (V_{\text{theoretical}} - V_{\text{measured}}) / V_{\text{theoretical}}$$

7. Comment on the measured behaviour of the DAC compared to ideal behaviour.

## REFERENCE

1. A.S. Sedra and K.S. Smith, "Microelectronic circuits", 5<sup>th</sup> ed., New York: Oxford University Press, 2004, 1283 p.